

Kevin Tavara

ECE-350-001

10.19.2020

Lab 4: Intelligent Lighting Controller

Description: The purpose of this lab is to create a dark sensor led circuit that will turn off in the light and on in the darkness while having some extra features such as outputting when the led was turned off or on and for how long has the led been turned off or on. The last feature is a push button switch that will act as a manual override button to manually set the led status.


Breadboard:

Red wire is to
pin 16

Black wire is
common
ground
connected to
pin 6

This blue wire is
connected to pin 12

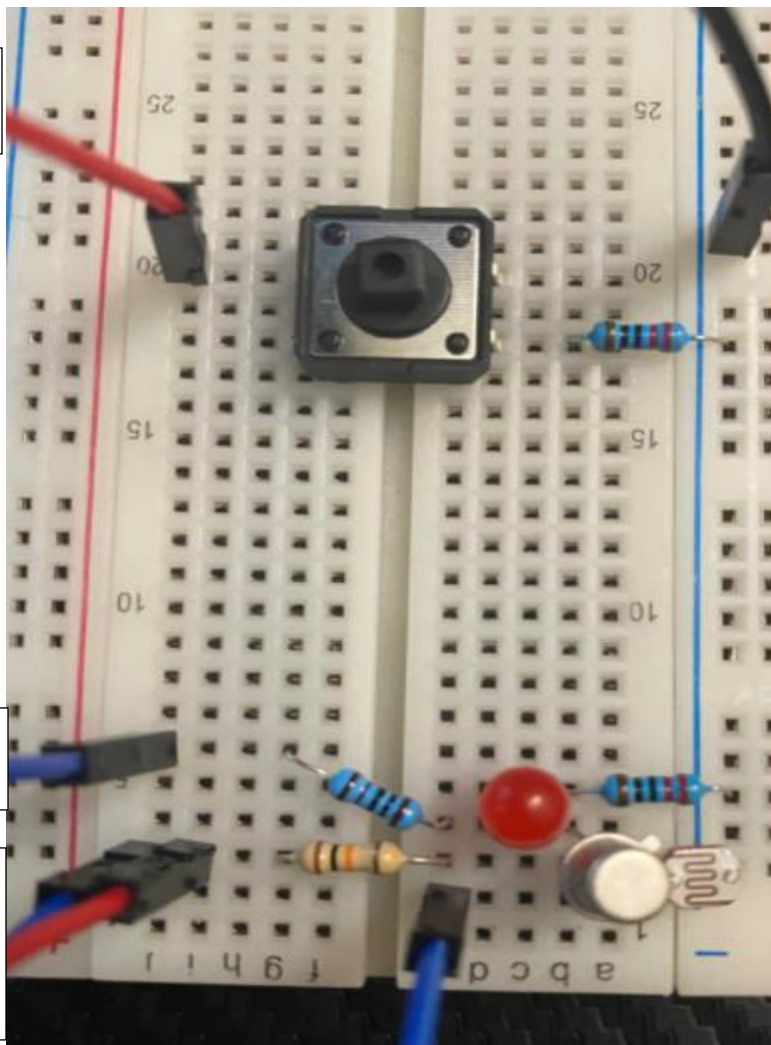Red wire is power for
transistor connected to pin
1. Blue wire extends power
to collector of transistor



Questions:

1. $R_{\max} = 8\sim 20\text{k}$ $R_{\min} = 1\text{M } \Omega$ $R_{\text{req}} = 10\text{k } \Omega$

2. We can input between + or $- 5\text{ mA}$